

---

# Sequential Circuit Analysis

---

Circuit Diagram to State Diagram  
State Diagram to Circuit Diagram  
Counters  
Application of Counters

---



# What is sequential logic

- ❑ Sequential circuit has additional dimension which is time
- ❑ Combinational logic only depends on current input
- ❑ Sequential circuit output depends on previous input other than current input
- ❑ More powerful than combination logic
- ❑ Able to model condition which can't be modeled by combinational logic



# Circuit Diagram to State Diagram

---

# Example 1: Draw the state diagram for the given circuit

Sequential circuit using D flip flop

**Present States:**

A and B

**Input:**


DA, DB, x

**Next States:**

A+ and B+

**Output:**

y

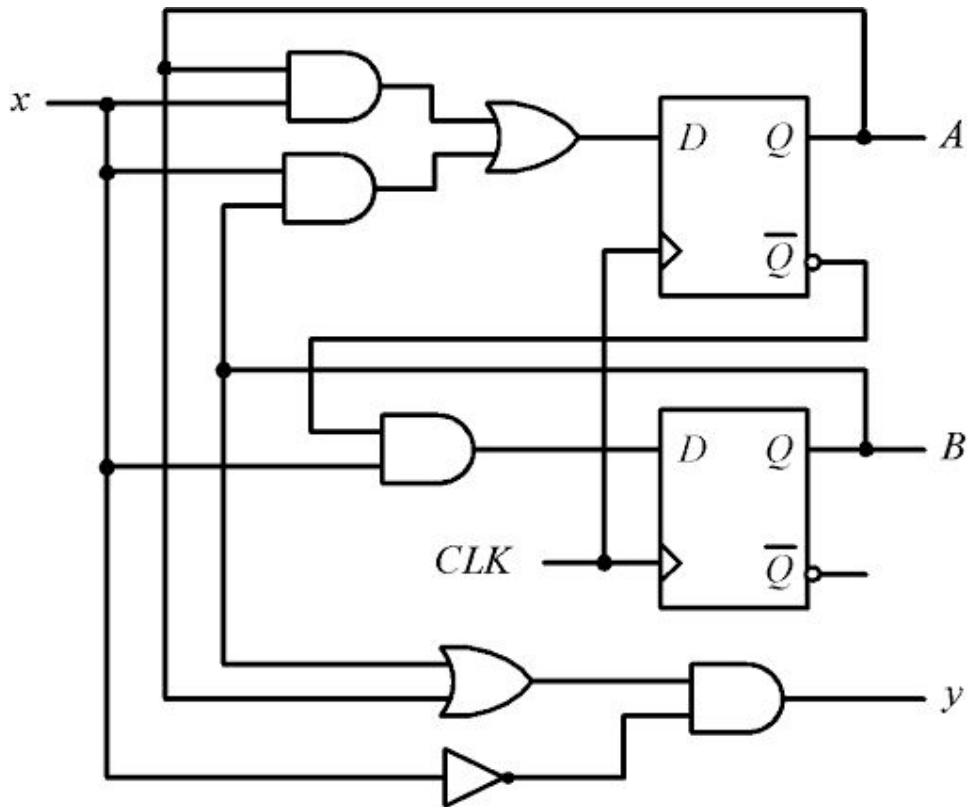


# Example 1: Draw the state diagram for the given circuit

1. Find out the input equations of the flip flop and the output equation

$$DA = Ax + Bx$$

$$DB = A'x$$

$$y = (A+B)x'$$

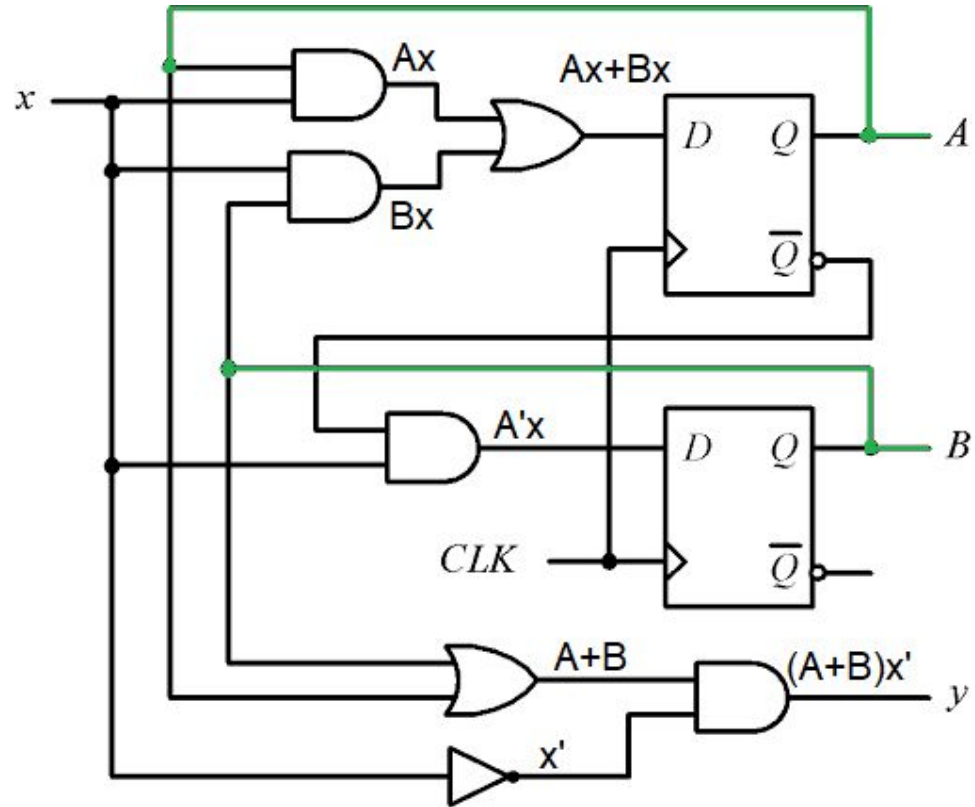

# Example 1: Draw the state diagram for the given circuit

2. Construct the state table according to the flip flop input and output equations

$$DA = Ax + Bx$$

$$DB = A'x$$

$$y = (A+B)x'$$

When A=0, B=0, x=0,

$$DA = 0.0 + 0.0 = 0$$

$$DB = 0'.0 = 0$$

$$y = (0+0).0' = 0$$

When A=0, B=0, x=1,

$$DA = 0.1 + 0.1 = 0$$

$$DB = 0'.1 = 1$$

$$y = (0+0).1' = 0$$

A	B	x	DA	DB	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

# Example 1: Draw the state diagram for the given circuit

3. Find out the next states from the flip flop input values

## D Flip-flop Truth table

D	Q
0	0
1	1

$$\therefore DA = A+$$

$$\therefore DB = B+$$


A	B	x	DA	DB	y	A+	B+
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	1
0	1	0	0	0	1	0	0
0	1	1	1	1	0	1	1
1	0	0	0	0	1	0	0
1	0	1	1	0	0	1	0
1	1	0	0	0	1	0	0
1	1	1	1	0	0	1	0



## Example 1: Draw the state diagram for the given circuit

A	B	x	A+	B+	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

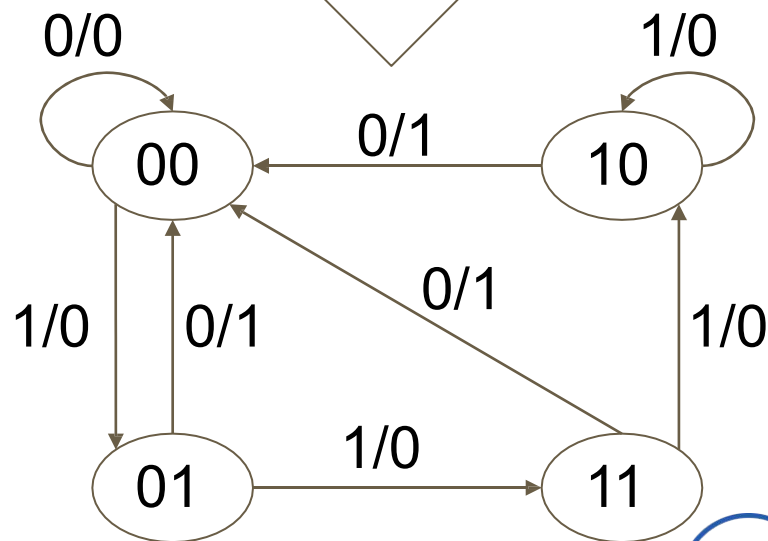4. Draw the state diagram from the state table



State Diagram



## Example 2: Draw the state diagram for the given circuit

## Sequential circuit using JK flip flop

## Present States:

A and B

**Input:**


JA, KA, JB, KB, x

## Next

### States:

A+ and B+


## Sequential circuit using JK flip flop

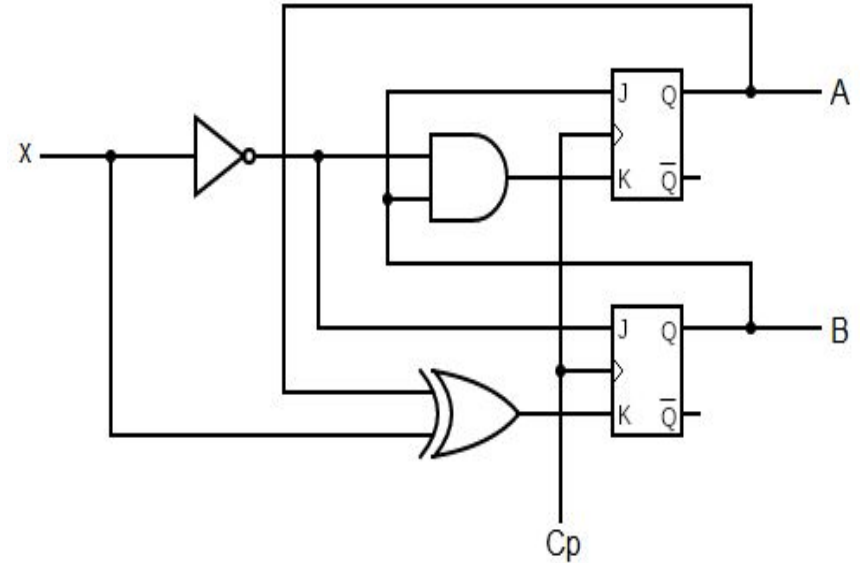

# Example 2: Draw the state diagram for the given circuit

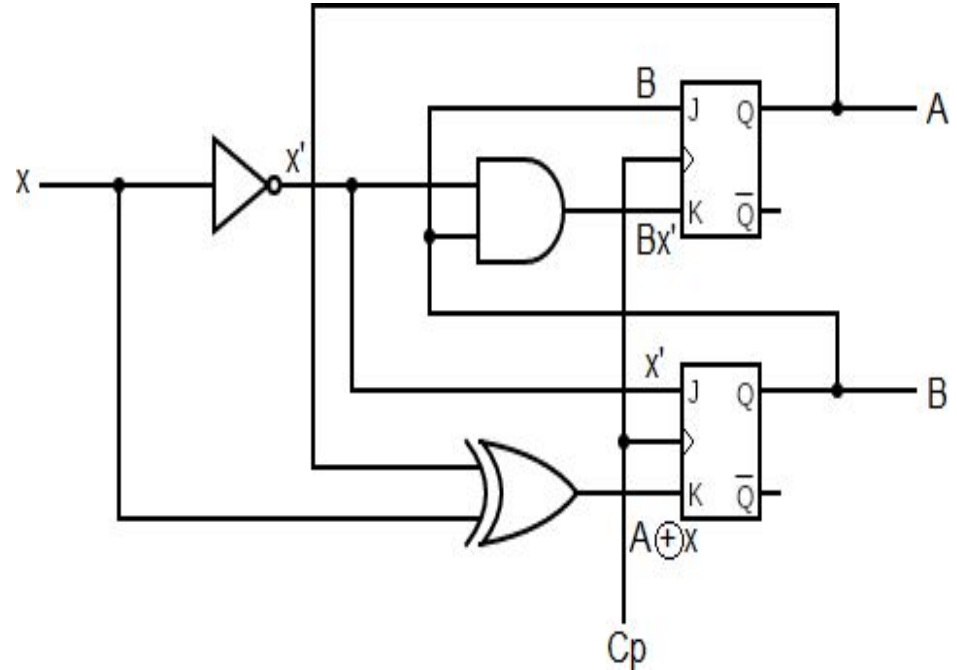1. Find out the input equations of the flip flop and the output equation

$$\begin{aligned} \mathbf{JA} &= \mathbf{B} \\ \mathbf{KA} &= \mathbf{Bx'} \\ \mathbf{JB} &= \mathbf{x'} \\ \mathbf{KB} &= \mathbf{A \text{ xor } X} \end{aligned}$$



## Example 2: Draw the state diagram for the given circuit

2. Construct the state table according to the flip flop input and output equations

$$\begin{aligned} \mathbf{JA} &= \mathbf{B} \\ \mathbf{KA} &= \mathbf{Bx'} \\ \mathbf{JB} &= \mathbf{x'} \\ \mathbf{KB} &= \mathbf{A \text{ xor } X} \end{aligned}$$

When  $A=0, B=0, x=0$ ,

$$JA = 0$$

$$KA = 0.0' = 0$$

$$JB = 0' = 1$$

$$KB = 0 \text{ xor } 0 = 0$$

When  $A=0, B=0, x=1$ ,

$$JA = 0$$

$$KA = 0.1' = 0$$

$$JB = 1' = 0$$

$$KB = 0 \text{ xor } 0 = 0$$

A	B	x	JA	KA	JB	KB
0	0	0	0	0	1	0
0	0	1	0	0	0	1
0	1	0	1	1	1	0
0	1	1	1	0	0	1
1	0	0	0	0	1	1
1	0	1	0	0	0	0
1	1	0	1	1	1	1
1	1	1	1	0	0	0

## Example 2: Draw the state diagram for the given circuit

3. Find out the next states from the flip flop input values

A	B	x	JA	KA	JB	KB	A+	B+
0	0	0	0	0	1	0	0	1
0	0	1	0	0	0	1	0	0
0	1	0	1	1	1	0	1	1
0	1	1	1	0	0	1	1	0
1	0	0	0	0	1	1	1	1
1	0	1	0	0	0	0	1	0
1	1	0	1	1	1	1	0	0
1	1	1	1	0	0	0	1	1


### JK Flip-flop Truth table

J	K	Q
0	0	Memory/ No change
0	1	0
1	0	1
1	1	Toggle

## Example 2: Draw the state diagram for the given circuit

A	B	x	A+	B+
0	0	0	0	1
0	0	1	0	0
0	1	0	1	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	1

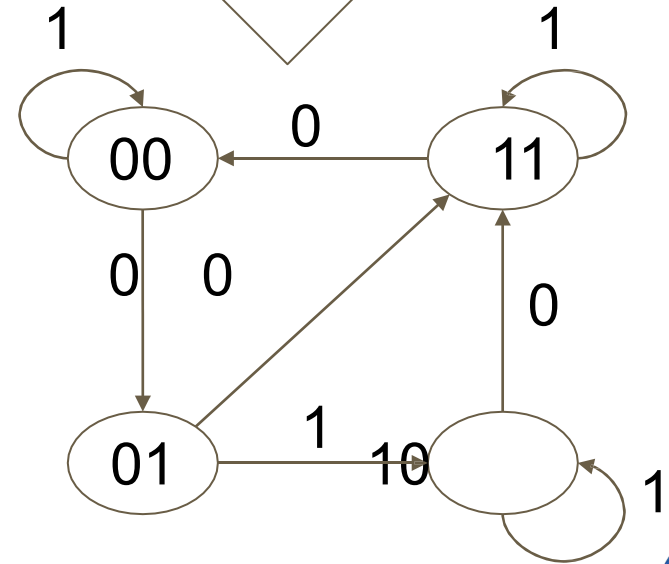4. Draw the state diagram from the state table



State Diagram


# State Diagram to Circuit Diagram

---
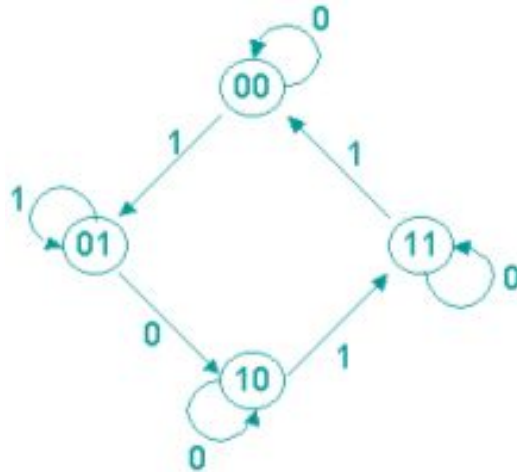
# Design: Example 1


---

Given state diagram as follows, get the sequential circuit using JK flip-flop


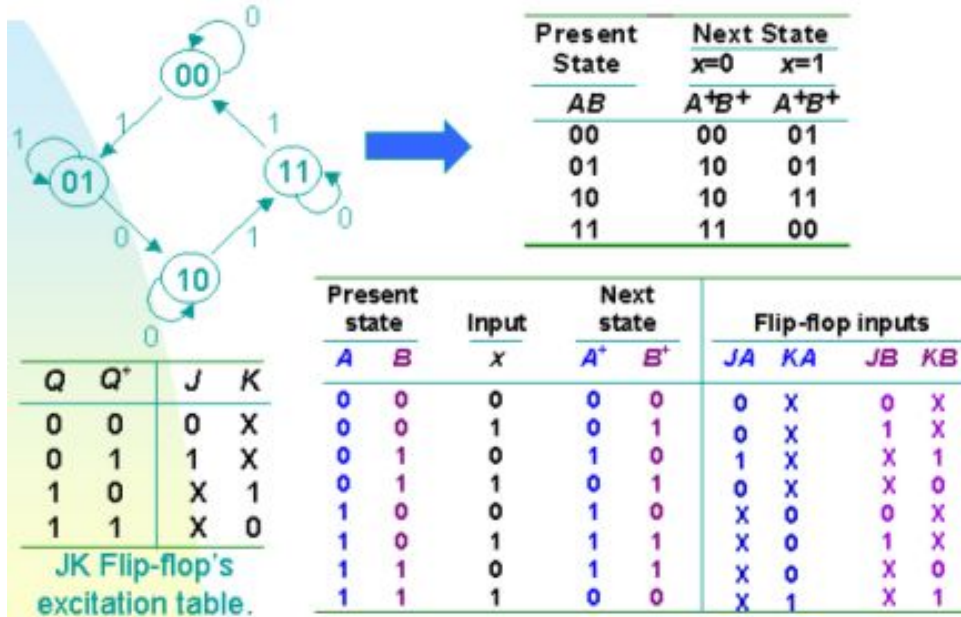
# Design: Example 1

State/excitation table using JK flip-flop



Note:

**Step 1:** Build state table

**Step 2:** Find no. of Flip-Flop (i.e.  $2^m$  states means  $m$  flip-flops)

**Step 3:** Build Excitation table

**Step 4:** Use K-map to find input functions

**Step 5:** Design logic diagram



# Design: Example 1

From state table, get input flip-flop function

Present state		Input $x$	Next state		Flip-flop inputs			
$A$	$B$		$A^+$	$B^+$	$JA$	$KA$	$JB$	$KB$
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

Karnaugh map for  $JA$ . The map shows a 1 in the cell for  $A=0, B=1, x=0$  and X's in the other cells for  $A=0$ . The expression is  $JA = B.x'$ .

Karnaugh map for  $KA$ . The map shows X's in the cells for  $A=0, B=0, x=0$  and  $A=0, B=0, x=1$ , and a 1 in the cell for  $A=0, B=1, x=1$ . The expression is  $KA = B.x$ .

Karnaugh map for  $JB$ . The map shows 1's in the cells for  $A=0, B=0, x=1$  and  $A=0, B=1, x=1$ , and X's in the other cells. The expression is  $JB = x$ .

Karnaugh map for  $KB$ . The map shows X's in the cells for  $A=0, B=0, x=0$  and  $A=0, B=1, x=0$ , and 1's in the cells for  $A=0, B=0, x=1$  and  $A=0, B=1, x=1$ . The expression is  $KB = (A \oplus x)'$ .


# Design: Example 1

Input flip-flop function

$$\begin{aligned}JA &= B.x' \\KA &= B.x\end{aligned}$$



$$\begin{aligned}JB &= x \\KB &= (A \oplus x)'\end{aligned}$$

Logic Diagram

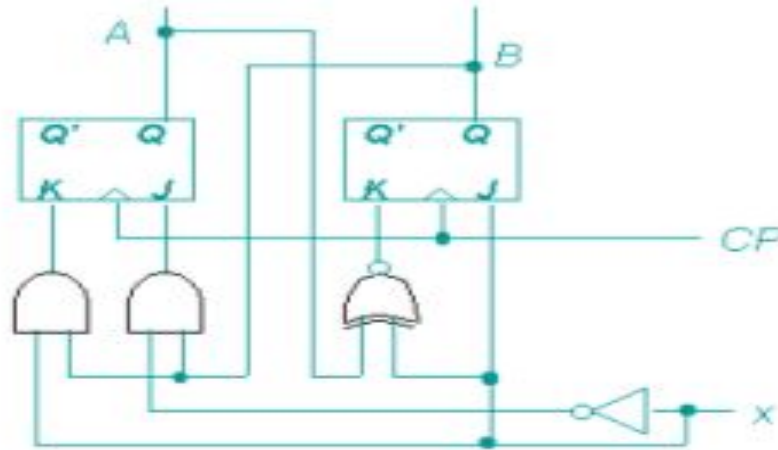
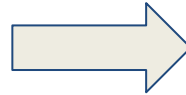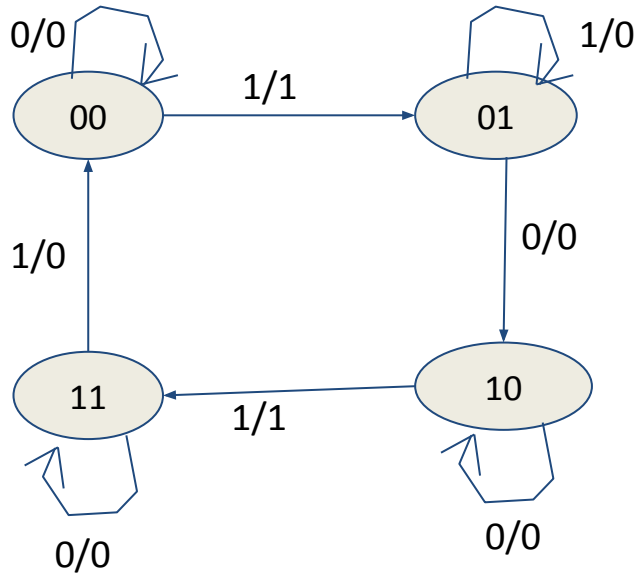
# Design: Example 2

Design, using D flip-flop, circuit is based on state table below. (Exercise: How if using JK flip-flop)



Present state		Input $x$	Next state		Output $y$
$A$	$B$		$A^+$	$B^+$	
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	1	1	0
1	1	1	0	0	0


# Design: Example 2

Determine input expression for flip-flop and y output

A	B	x	A+	B+	y	DA	DB
0	0	0	0	0	0	0	0
0	0	1	0	1	1	0	1
0	1	0	1	0	0	1	0
0	1	1	0	1	0	0	1
1	0	0	1	0	0	1	0
1	0	1	1	1	1	1	1
1	1	0	1	1	0	1	1
1	1	1	0	0	0	0	0


Q	Q <sup>+</sup>	D
0	0	0
0	1	1
1	0	0
1	1	1

D Flip-flop

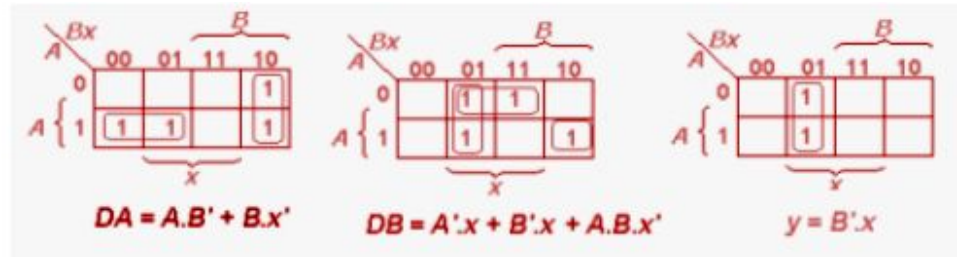
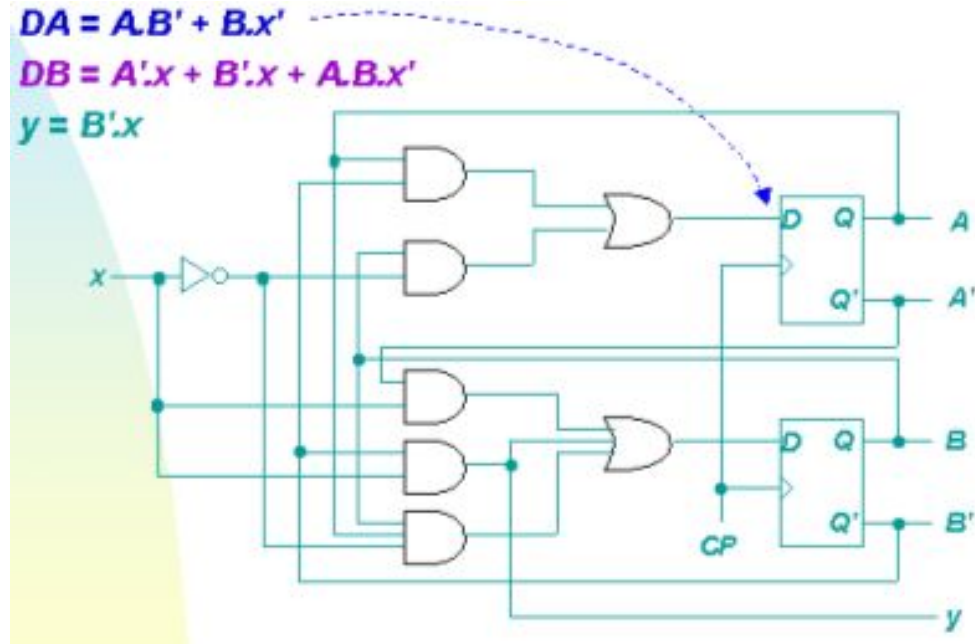
# Design: Example 2

From expression built, draw logic diagram



# Introduction: Counters

- **Counters** are circuits that cycle through a specified number of states.
- Two types of counters:
  - ❖ synchronous (parallel) counters
  - ❖ asynchronous (ripple) counters
- Ripple counters allow some flip-flop outputs to be used as a source of clock for other flip-flops.
- Synchronous counters apply the same clock to all flip-flops.
- **We will cover only synchronous this time**


# Synchronous (Parallel) Counters

- **Synchronous (parallel) counters:** the flip-flops are clocked at the same time by a common clock pulse.
- We can design these counters using the sequential logic design process.
- Example: 2-bit synchronous binary counter (using T flip-flops, or JK flip-flops with identical J,K inputs).

# Synchronous (Parallel) Counters

Question: Design a 2-bit synchronous binary counter (using T flip-flops).

Start by drawing this

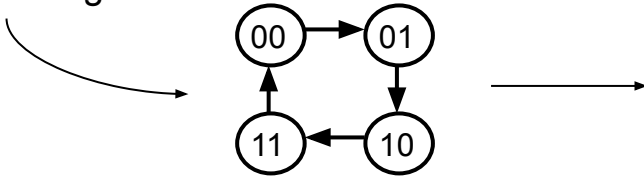

$Q_n$	$Q_{n+1}$	T
0	0	0
0	1	1
1	0	1
1	1	0

*Excitation table of T flip flop*

Present state		Next state		Flip-flop inputs	
$A_1$	$A_0$	$A_1^+$	$A_0^+$	$TA_1$	$TA_0$
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1



# Synchronous (Parallel) Counters


Present state		Next state		Flip-flop inputs	
$A_1$	$A_0$	$A_1^+$	$A_0^+$	$TA_1$	$TA_0$
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1

Next, find out the equations for the flip-flop inputs.

$$TA_1 = A_1'A_0 + A_1A_0 = A_0(A_1' + A_1) = A_0$$

$$TA_0 = 1$$

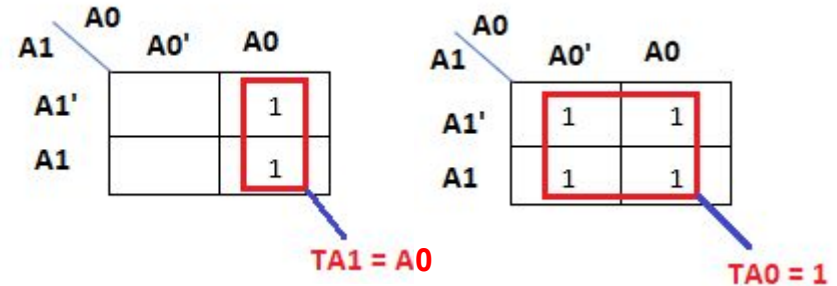FYI, these can also be calculated using K-Maps




# Synchronous (Parallel) Counters

$$TA_1 = A_1'A_0 + A_1A_0 = A_0(A_1' + A_1) = A_0$$

$$TA_0 = 1$$


Finally draw the circuit diagram

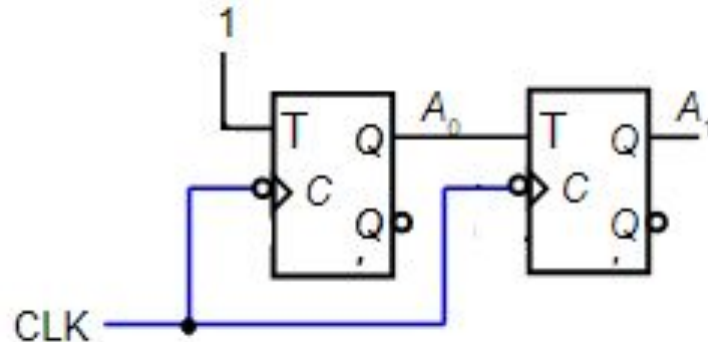

# Synchronous (Parallel) Counters

Start by drawing this

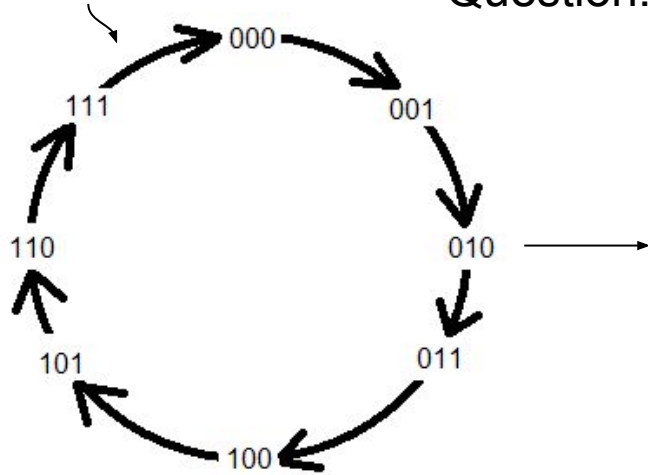
- Question: Design a 3-bit synchronous binary counter (using T).



Present state			Next state			Flip-flop inputs		
$A_2$	$A_1$	$A_0$	$A_2^+$	$A_1^+$	$A_0^+$	$TA_2$	$TA_1$	$TA_0$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

$Q_n$	$Q_{n+1}$	T
0	0	0
0	1	1
1	0	1
1	1	0

Excitation table of T flip-flop

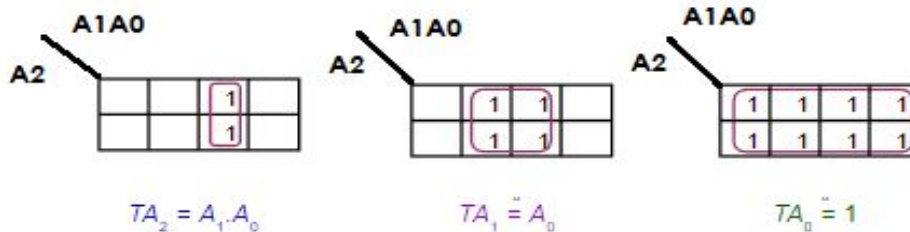


FYI, these can also be calculated using Boolean simplifications
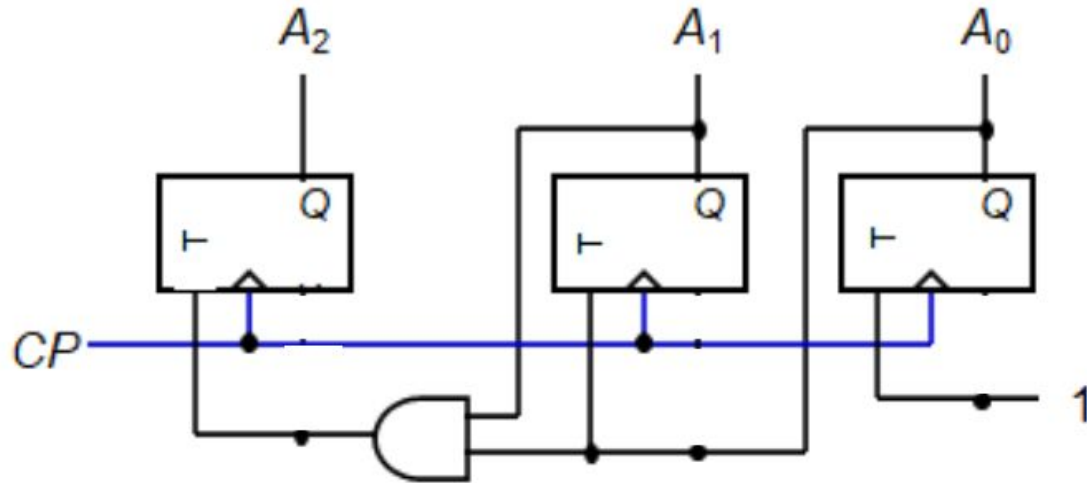
# Synchronous (Parallel) Counters

Draw the circuit diagram

$$TA_2 = A_1 \cdot A_0 \quad TA_1 = A_0 \quad TA_0 = 1$$



# Self-Study

## 4 bit synchronous up counter


- Equations and diagram will look like the following:

$$TA_3 = A_2 \cdot A_1 \cdot A_0$$

$$TA_2 = A_1 \cdot A_0$$

$$TA_1 = A_0$$

$$TA_0 = 1$$

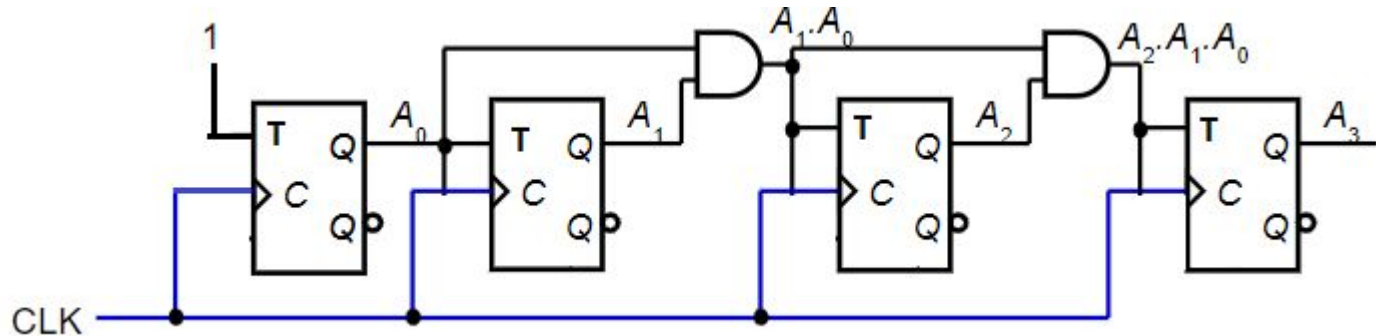


# Up/Down Synchronous Counters

- **Up/down synchronous counter**: a *bidirectional* counter that is capable of counting either up or down.
- An input (control) line *Up/Down* (or simply *Up*) specifies the direction of counting.
  - ❖  $\overline{Up/Down} = 0 \rightarrow$  Count upward
  - ❖  $Up/Down = 1 \rightarrow$  Count downward

# 3 bit Synchronous Up/Down Counter

U/D	Present states			Next States			Flipflop inputs		
M	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>2</sub> <sup>+</sup>	Q <sub>1</sub> <sup>+</sup>	Q <sub>0</sub> <sup>+</sup>	TQ <sub>2</sub>	TQ <sub>1</sub>	TQ <sub>0</sub>
0	0	0	0	0	0	1	0	0	1
0	0	0	1	0	1	0	0	1	1
0	0	1	0	0	1	1	0	0	1
0	0	1	1	1	0	0	1	1	1
0	1	0	0	1	0	1	0	0	1
0	1	0	1	1	1	0	0	1	1
0	1	1	0	1	1	1	0	0	1
0	1	1	1	0	0	0	1	1	1
1	0	0	0	1	1	1	1	1	1
1	0	0	1	0	0	0	0	0	1
1	0	1	0	0	0	1	0	1	1
1	0	1	1	0	1	0	0	0	1
1	1	0	0	0	1	1	1	1	1
1	1	0	1	1	0	0	0	0	1
1	1	1	0	1	0	1	0	1	1
1	1	1	1	1	1	0	0	0	1

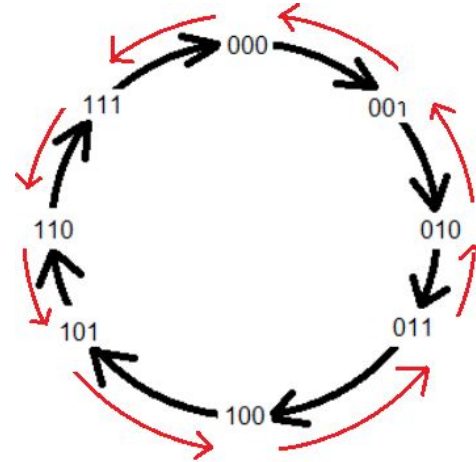


Q <sub>n</sub>	Q <sub>n+1</sub>	T
0	0	0
0	1	1
1	0	1
1	1	0


Excitation table of T flip flop

U/D	Present states			Next States			Flipflop inputs		
M	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>2</sub> +	Q <sub>1</sub> +	Q <sub>0</sub> +	TQ <sub>2</sub>	TQ <sub>1</sub>	TQ <sub>0</sub>
0	0	0	0	0	0	1	0	0	1
0	0	0	1	0	1	0	0	1	1
0	0	1	0	0	1	1	0	0	1
0	0	1	1	1	0	0	1	1	1
0	1	0	0	1	0	1	0	0	1
0	1	0	1	1	1	0	0	1	1
0	1	1	0	1	1	1	0	0	1
0	1	1	1	0	0	0	1	1	1
1	0	0	0	1	1	1	1	1	1
1	0	0	1	0	0	0	0	0	1
1	0	1	0	0	0	1	0	1	1
1	0	1	1	0	1	0	0	0	1
1	1	0	0	0	1	1	1	1	1
1	1	0	1	1	0	0	0	0	1
1	1	1	0	1	0	1	0	1	1
1	1	1	1	1	1	0	0	0	1


## 3 bit Synchronous Up/Down Counter

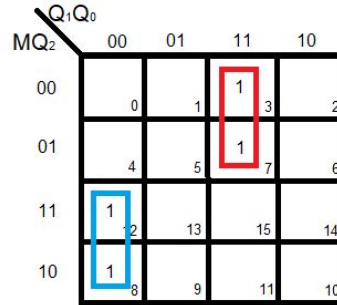

$$TQ_2 = M'Q_1Q_0 + MQ_1'Q_0'$$

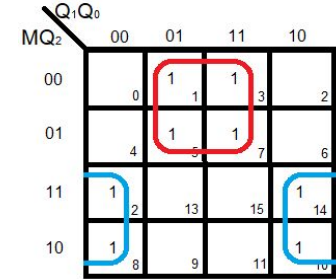

$$TQ_1 = M'Q_0 + MQ_0'$$

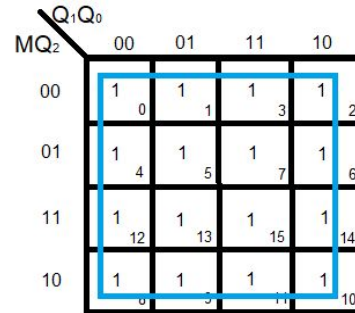


$$TQ_0 = 1$$


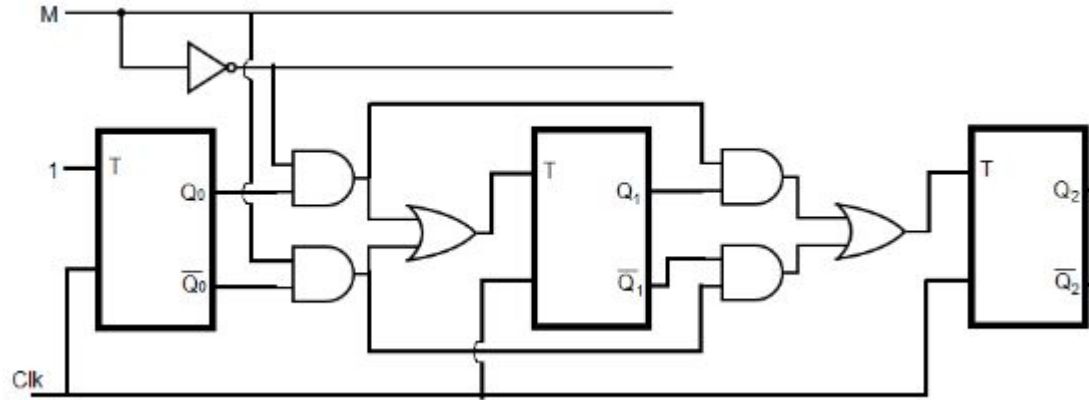
## 3 bit Up/Down Synchronous Counter

Draw the circuit diagram

(The number of present state will be equal to the number of flip-flops in the circuit)




# Practice Problem using Counters

# PRACTICE PROBLEM - 1

- Implement the following counter using T FF: 1-→2-→3-→5-→7-→11-→13-→1

Start by drawing this

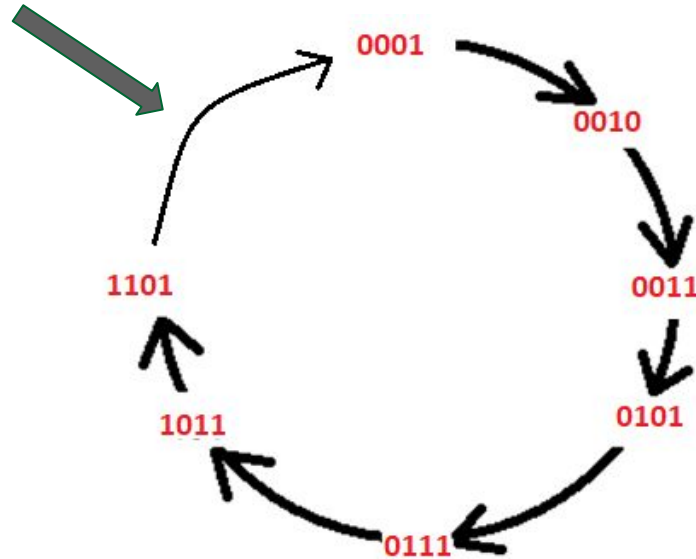

Present states				Next States				Flip-flop inputs			
A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>	A <sub>3</sub> +	A <sub>2</sub> +	A <sub>1</sub> +	A <sub>0</sub> +	TA <sub>3</sub>	TA <sub>2</sub>	TA <sub>1</sub>	TA <sub>0</sub>
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	0	1	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	1
0	0	1	1	0	1	0	1	0	1	1	0
0	1	0	0	0	0	0	1	0	1	0	1
0	1	0	1	0	1	1	1	0	0	1	0
0	1	1	0	0	0	0	1	0	1	1	1
0	1	1	1	1	0	1	1	1	1	0	0
1	0	0	0	0	0	0	1	1	0	0	1
1	0	0	1	0	0	0	1	1	0	0	0
1	0	1	0	0	0	0	1	1	0	1	1
1	0	1	1	1	1	0	1	0	1	1	0
1	1	0	0	0	0	0	1	1	1	0	1
1	1	0	1	0	0	0	1	1	1	0	0
1	1	1	0	0	0	0	1	1	1	1	1
1	1	1	1	0	0	0	1	1	1	1	0

Q <sub>n</sub>	Q <sub>n+1</sub>	T
0	0	0
0	1	1
1	0	1
1	1	0

*Excitation table of T flip flop*

For present states not mentioned in the question, next state will be the INITIAL STATE [0001 in this question]. It's important to show the states that are not mentioned in the question. Otherwise, the circuit will stop working if any of those states show up.

Present states				Next States				Flip-flop inputs			
A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>	A <sub>3</sub> <sup>+</sup>	A <sub>2</sub> <sup>+</sup>	A <sub>1</sub> <sup>+</sup>	A <sub>0</sub> <sup>+</sup>	TA <sub>3</sub>	TA <sub>2</sub>	TA <sub>1</sub>	TA <sub>0</sub>
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	0	1	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	1
0	0	1	1	0	1	0	1	0	1	1	0
0	1	0	0	0	0	0	1	0	1	0	1
0	1	0	1	0	1	1	1	0	0	1	0
0	1	1	0	0	0	0	1	0	1	1	1
0	1	1	1	1	0	1	1	1	1	0	0
1	0	0	0	0	0	0	1	1	0	0	1
1	0	0	1	0	0	0	1	1	0	0	0
1	0	1	0	0	0	0	1	1	0	1	1
1	0	1	1	1	1	0	1	0	1	1	0
1	1	0	0	0	0	0	1	1	1	0	1
1	1	0	1	0	0	0	1	1	1	0	0
1	1	1	0	0	0	0	1	1	1	1	1
1	1	1	1	0	0	0	1	1	1	1	0

A1A0

A3A2 \ A1A0	A1'A0'	A1'A0	A1A0	A1A0'
A3'A2'				
A3'A2			1	
A3A2	1	1	1	1
A3A2'	1	1		1

$$TA_3 = A_3A_0' + A_3A_1' + A_2A_1A_0$$

A1A0

A3A2 \ A1A0	A1'A0'	A1'A0	A1A0	A1A0'
A3'A2'			1	
A3'A2	1		1	1
A3A2	1	1	1	1
A3A2'			1	

$$TA_2 = A_2A_0' + A_3A_2 + A_1A_0$$

Present states				Next States				Flip-flop inputs			
A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>	A <sub>3</sub> <sup>+</sup>	A <sub>2</sub> <sup>+</sup>	A <sub>1</sub> <sup>+</sup>	A <sub>0</sub> <sup>+</sup>	TA <sub>3</sub>	TA <sub>2</sub>	TA <sub>1</sub>	TA <sub>0</sub>
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	0	1	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	1
0	0	1	1	0	1	0	1	0	1	1	0
0	1	0	0	0	0	0	1	0	1	0	1
0	1	0	1	0	1	1	1	0	0	1	0
0	1	1	0	0	0	0	1	0	1	1	1
0	1	1	1	1	0	1	1	1	1	0	0
1	0	0	0	0	0	0	1	1	0	0	1
1	0	0	1	0	0	0	1	1	0	0	0
1	0	1	0	0	0	0	1	1	0	1	1
1	0	1	1	1	1	0	1	0	1	1	0
1	1	0	0	0	0	0	1	1	1	0	1
1	1	0	1	0	0	0	1	1	1	0	0
1	1	1	0	0	0	0	1	1	1	1	1
1	1	1	1	0	0	0	1	1	1	1	0

A1A0

A3A2 \ A1A0	A1'A0'	A1'A0	A1A0	A1A0'
A3'A2'		1	1	
A3'A2		1		1
A3A2			1	1
A3A2'			1	1

$$TA_1 = A_3'A_1'A_0 + A_3'A_2'A_0 + A_2A_1A_0' + A_3A_1$$

A1A0

A3A2 \ A1A0	A1'A0'	A1'A0	A1A0	A1A0'
A3'A2'	1	1		1
A3'A2	1			1
A3A2	1			1
A3A2'	1			1

$$TA_0 = A_0' + A_3'A_2'A_1$$

$$\begin{aligned}
 TA3 &= A3A0' + A3A1' + A2A1A0 \\
 TA2 &= A2A0' + A3A2 + A1A0 \\
 TA1 &= A3'A1'A0 + A3'A2'A0 + A2A1A0' + A3A1 \\
 TA0 &= A0' + A3'A2'A1'
 \end{aligned}$$

Draw the circuit yourself

# PRACTICE PROBLEM - 2

- Implement the following counter using D FF: Green->Yellow->Red->Yellow->Green

Let's assume: Green = 00, Yellow = 01, Red = 10

Present states			Next States		Flip-flop inputs	
A	B	x	A+	B+	DA	DB
0	0	0	0	1	0	1
0	0	1	0	1	0	1
0	1	0	0	0	0	0
0	1	1	1	0	1	0
1	0	0	0	1	0	1
1	0	1	0	1	0	1
1	1	0	x	x	x	x
1	1	1	x	x	x	x

Find out the equations for the flip-flop inputs

$$DA = Bx$$

$$DB = B'$$

$Q_n$	$Q_{n+1}$	D
0	0	0
0	1	1
1	0	0
1	1	1

Excitation table of D flip flop

Special Note: You may need to use more than 1 external input depending upon the question.



Draw the circuit diagram (The number of present state will be equal to the number of flip-flops in the circuit)

