

Department of Computer Science and Engineering
BRAC University
CSE 260: Digital Logic Design

Experiment # 3

Parity Generator and Checker

Objective:


- To design and implement an Even parity Generator and Even parity checker using XOR gates (IC-7486).

Required Components and Equipments


1. AT-700 Portable Analog/Digital Laboratory
2. 7486

Diagram of Circuit:

Even Parity generator

 

Even Parity Checker

 

Procedure:

- Construct the Circuit of Figure 1, on the breadboard of AT-700.
 - Remember each IC's pin 14 connected to "+5V" position of DC Power Supply of AT-700, and pin 7 connected to "GND" position.
 - Connect the inputs to Data switches and outputs to any position of LED Display.
-
- Determine the parity generator's output for each of the following sets of input data, $D_3D_2D_1D_0$; (a) 0111; (b) 1001; (c) 0000; (d) 0100

- Determine the parity checker's output for each of the following sets of data from the transmitter

P	D_3	D_2	D_1	D_0	Error (E)
0	1	0	1	0	
1	1	1	1	0	
1	1	1	1	1	
1	0	0	0	0	

Report:

The report should cover the followings

1. Name of the Experiment
2. Objective
3. Required Components and Equipments
4. Experimental Setup (You must draw the diagrams)
5. Results in Tabulated form (Create table for truth table generator and checker).
6. Discussions (Explanation of the results)