

Department of Computer Science and Engineering
BRAC University
CSE 260: Digital Logic Design

Experiment # 2

Universal Gates and Applications of Boolean algebra

Objective:

- To investigate the rules of Boolean algebra.
- To gain experience working with practical circuits
- To simplify a complex function using Boolean algebra

Required Components and Equipments

1. AT-700 Portable Analog/Digital Laboratory
2. 7400×1




Mandatory Readings:

BOOLEAN THEOREMS

1. $x.0=0$
2. $x.1=x$
3. $x.x=x$
4. $x.\bar{x}=0$
5. $x+0=x$
6. $x+1=1$
7. $x+x=x$
8. $x + \bar{x} = 1$
9. $x+y=y+x$ (Commutative laws)
10. $x.y=y.x$ (Commutative laws)
11. $x+(y+z)=(x+y)+z=x+y+z$ (Associative laws)
12. $x(yz)=(xy)z=xyz$ (Associative laws)
13. $(w+x)(y+z)=wy+xy+wz+xz$
14. $x+xy=x$
15. $x + \bar{x}y = x + y$
16. $\bar{x} + xy = \bar{x} + y$
17. $\overline{x + y} = \bar{x}.\bar{y}$ (DeMorgan's Theorem)
18. $\overline{x.y} = \bar{x} + \bar{y}$ (DeMorgan's Theorem)

Diagram of Circuit:

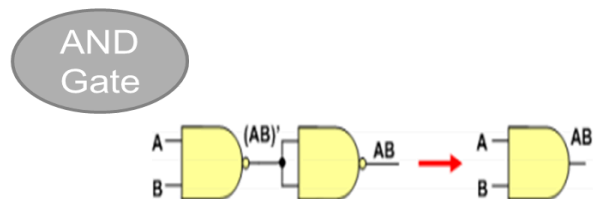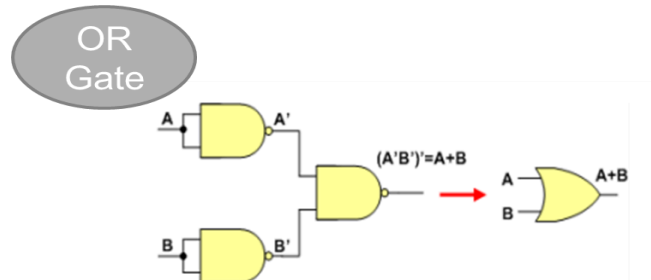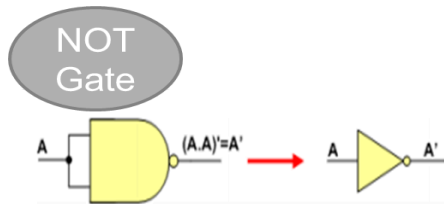Building Basic Gates using Universal [NAND] Gates:



Building Basic Gates using Universal [NOR] Gates:

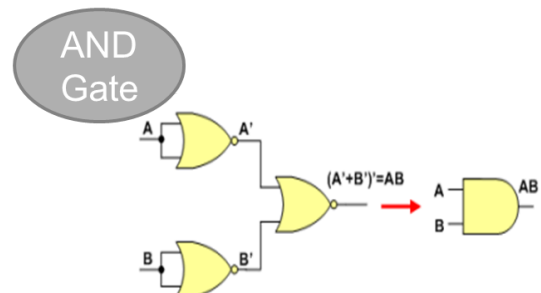
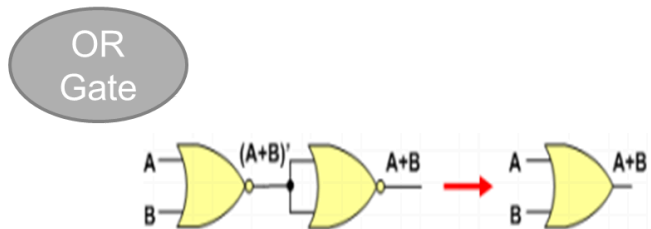
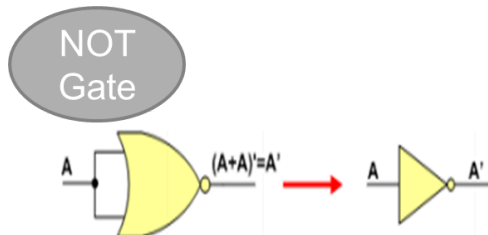


Diagram 1: Building Circuit using Universal Gates [NAND]:


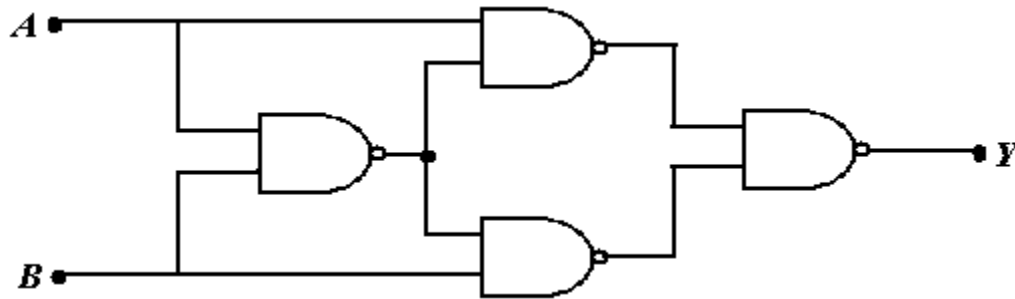


Diagram 2: Building Circuit using Universal Gates [NOR]:

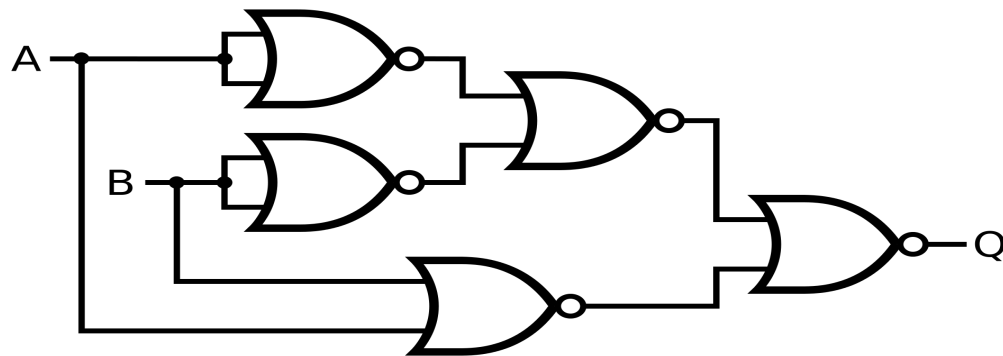

Procedure:

- Construct the Circuit of Figure 1, on the breadboard of AT-700.
- Remember each IC's pin 14 connected to "+5V" position of DC Power Supply of AT-700, and pin 7 connected to "GND" position.
- Connect the inputs to Data switches and outputs to any position of LED Display.
- Find out the outputs for all possible combinations of input states.
- Write down the input-output in tabular form.

Report:

The report should cover the followings

1. Name of the Experiment
2. Objective
3. Required Components and Equipments
4. Experimental Setup (Draw diagram 1 and 2)
5. Results (Truth Table) and Discussions .The discussions part must include the answers of the following questions:
 - What is the Boolean Equation for the output (for both diagrams)?
 - Simplify the Boolean equations (for both diagrams).
 - The circuits' functions are identical to two single gates. Write down the name of those gates.
 - Implement the following function using NAND gate only: $(A(AB+CD))'$. Do not simplify the function. Draw the diagram only.